



Figure 1 A piezoelectric ceramic buzzer serves as the oscillator in this flyback supply that lights a white LED using a single cell (not shown).