



Figure A This battery simulator has a floating output settable within 1 mV. A₁ unloads the Kelvin-Varley divider, and A₂ buffers the capacitive load.