



**Figure B** The 150-k $\Omega$ -resistor/1- $\mu$ F-capacitor compensation network provides clean response despite a 680- $\mu$ F output capacitor.

---