



Figure A This unworkable scheme suppresses high common-mode voltages by converting cell potentials to current. The circuit decodes amplifier outputs to derive individual cell voltages. The required resistor precision and values are unrealistic. In addition, the resistors draw current from the cells.