



Figure C This switched-capacitor scheme rejects common-mode voltage but requires high-voltage switches, nonoverlapping drive, and a level shift. The switch leakage degrades accuracy. Optically driven switches can simplify the level shift, but breakdown and leakage issues remain.