



Figure 1 The N-channel MOSFET and zener diode protect the switching regulator against transient voltages as high as 50V in automotive applications.