



Figure 1 This RTD circuit uses a second-order polynomial to linearize the output of the sensor.