



Figure 1 In these simple circuits, the LEDs need a voltage of approximately 1.5V (a) or more than 5V (b) to turn on. The circuits allow a battery-powered microcontroller to control two LEDs with only one I/O pin.