



Figure 1 A quad optoisolator arranged in a full-wave analog-multiplier bridge senses and calculates watts of ac-power consumption and ignores any reactive component in the load.