



Figure 1 Using only one I/O pin, this circuit and a simple program can sense the state of a three-position switch.