



Figure 1 Adding  $R_{IN}$  to this bandpass filter based on a TQE structure causes the circuit to show high input impedance.