



Figure 1 This single-stage transformer-flyback topology for an external power supply operates from ac line voltage but has a different switching control that directly gives an isolated low-voltage output at a power factor of 0.9 or more.