



Figure 1 This circuit functions as a night-light. The LED stays off during daylight and turns on when the ambient light level drops.