



Figure 1 An op amp has a conventional gain of -10 . The noise gain is 11, so all of the input errors appear at the output with a gain of 11. You cannot distinguish the signal from noise just by looking at the output.