



Figure 1 If R_1 meets both the termination-impedance constraints (a) and the drive-current constraints (b), then both termination circuits perform equally well.