



Figure 3 You can map a simple, glitch-free multiplexer (a) with AND and OR gates that can create glitches (b).