



Figure 2 The conventional buck-boost architecture inverts the input voltage (a). You can see that the same circuit with a 5V input would work just as well, producing -4 and $-6V$ (b). Buck-boost circuits can also invert a negative voltage to a positive one (c).