



**Figure 3** The Ćuk buck-boost topology also inverts. It uses two inductors, which lower the fast-slewing currents into both the input and output capacitors.

---