



**Figure 5** The synchronous-H-bridge four-switch buck-boost converter also creates a positive voltage but with higher efficiency than the other architectures.

---