



**Figure 1** Using the 1-to-8 CD4051 analog demultiplexer you can interface a moving-dot LED display to a low-end microcontroller using just three outputs.