



Figure 2 An Atmel Tiny13 AVR microcontroller regulates two boost-dc/dc-converter outputs using its internal ADCs and PWMs.