



Figure 1 This circuit protects low-power laser diodes but is not suitable for higher-power laser diodes.