



Figure 1 A simple symbol represents an analog switch, but stray capacitances abound and small inductances occur because of the presence of bond wires (a). The on-resistance is variable with applied signal and power supply, and the capacitors also change with applied voltage (b).

---