



Figure 3 An electrical diagram of a four-transistor pixel has a fully pinned photo diode (a) that you can view in cross-section along with the transfer-gate transistor (b). In a typical timing diagram for a four-transistor pixel, the integration starts by activating the reset and transfer-gate transistors and setting the diode to its pinned potential (c).

