



Figure 1 Obtaining feedback from a low-voltage secondary winding, this high-voltage supply generates 500V with low quiescent current.