



Figure 1 This circuit integrates the mixer function with a noninverting amplifier. The two resistors in the feedback loop set the voltage-conversion gain.