



Figure 1 When fuse F₁ blows, the transistor biases on, sounding the buzzer and powering D₂.