



**Figure 1** In parallel with the cells of a battery-powered device, this analog circuit disconnects the battery after a delay. Touching contacts C and D with a finger turns on the switch, connecting the cells to the load. The components fit inside the battery compartment.