



Figure 3 This circuit addresses the problem of a lack of access to the negative contact of the battery holder. It is essentially the same as the circuit in Figure 2, except that you place Item A in series with the positive pole and attach B to the negative pole of the battery.