



Figure 1 This 8-bit, low-end microcontroller detects pulses from LEDs, yielding a simple tester.