



Figure 2 This circuit can control higher voltages because it supplements R_2 with a resistor to ground to form a voltage divider, ensuring that C_1 doesn't charge to a voltage that would destroy the gate of Q_1 .