



Figure 1 By adding counters and an oscillator to the output of a monostable multivibrator, you can generate any number of output-gate pulses.