



NOTE: D₁-D₄=1N6529.

Figure 11 This -1000V negative-output converter uses the controlled-transition-time feature of the LT1534. Amplifier A₁ provides low impedance, inverting feedback to the LT1534 IC.