



Figure 20 This 5V-powered transformer-coupled flyback converter produces a 350V output (courtesy Albert M Wu, Linear Technology).