



Figure 23 The duty-cycle-modulated operation of the circuit in Figure 22 shows that the high-voltage output (Trace B) ramps down until A_1 (Trace A) goes high. This approach enables the LT3468/T₁ to restore the output. The loop-repetition rate varies with input voltage, output set-point, and load.
