



Figure 25 The low-ripple output (Trace C) is apparent in the postregulator's operation. Traces A and B are the output of A_1 and Q_1 's collector, respectively. The blurring of the trace, right of the photo's center, derives from loop jitter.
