



NOTE: D_1 - D_4 =1SS306.

Figure 5 In this circuit, a switching regulator replaces the linearly operated current sink of Figure 4. This approach minimizes heating, although the output noise increases.