



Figure 6 The resonant Royer collector waveshape (Trace A) is similar to that of the previous circuits. An efficient, high-speed, switched-mode current-sink drive feeds inductor L_1 (Trace B).
