



Figure B You can add an ac-lead network for improved dynamic response. The diode clamps protect the feedback node from the capacitor's differentiated response.

---