



Figure C Adding a low-ripple, two-section filter slows the loop transmission, and the lead network provides stability. Resistor R sets the dc-output impedance.