



Figure 1 This simple astable multivibrator provides a low-cost way to drive an LED from a single cell.