



Figure 1 This circuit shows multiple Schmitt-trigger inverters functioning as a variety of set/reset toggles.