



Figure 1 By cascading an autozeroed instrumentation amplifier having a gain of  $2^3$  and instrumentation amplifiers having gains of five, you get a decade-gain instrumentation amp whose dc performance is much better than that of monolithic decade-gain instrumentation amps.