



Figure 1 This circuit provides a simple means of multiplexing the outputs of two 4017 counters for as many as 80 outputs.