



Figure 1 This ac controller borrows from a sigma-delta converter to output a number of whole cycles of ac-line power according to an input-control voltage.