



**Figure 1** A shunt regulator and associated circuitry function as a Schmitt trigger, lighting LED<sub>1</sub> when the battery is fully charged.