



**Figure 1** In this circuit,  $R_{IN}$  “isolates”  $C_{IN}$  from the op-amp output stage.  $C_{IN}$  provides a charge reservoir for the SAR ADC during the sampling period.

