



Figure 2 The open- and closed-loop-transfer function of the amplifier in Figure 1 does not contain R_{IN} and C_{IN} as loads.

