



BY BONNIE BAKER

## Do you question your sanity?

**H**ave you ever been in need of a second opinion when your sanity is at stake? The pulse oximeter may be able to provide that second opinion if your brain is oxygen-deprived. This condition could affect you if you are a pilot, hiking in the high altitude of a mountain range, or even undergoing surgery. The pulse oximeter is a noninvasive instrument that monitors SpO<sub>2</sub> (saturation of hemoglobin with oxygen) in your blood.

You measure the oxygen in the blood by alternating the on-times of a red LED with a 650-nm wavelength and an NIR (near-infrared) LED with a 940-nm wavelength, taking the ratio between the intensities from a photodiode, and comparing that ratio with an SpO<sub>2</sub> look-up table in the microcontroller (Reference 1).

The transimpedance amplifier appears in medical and laboratory instrumentation, position and proximity sensors, photographic analyzers, bar-code scanners, and even smoke detectors. In the medical field, you will primarily find transimpedance amplifiers in the CT (computed-tomography)-scanner front end and the pulse oximeter. Figure 1 shows a simplified block diagram of a pulse oximeter (Reference 2).

In the circuit in Figure 1, the red LED is on for 50  $\mu$ sec, both LEDs are off for 450  $\mu$ sec, the NIR LED is on for 50  $\mu$ sec, and then both LEDs are off for 450  $\mu$ sec. The system repeats this cycle continuously. The transimpedance amplifier, A<sub>1</sub>, converts the photodiode current generated by the LEDs to a voltage at the output. The signal then travels through a bandpass filter and gain stage to the 12-bit ADC. The signal also travels through a low-pass filter to regulate the driver power to the LEDs. The microcontroller acquires the signals from the 12-bit ADC, computes the ratio of the red- and NIR-LED signals, and compares the results with a look-up table. The LCD shows a percentage of oxygenated hemoglobin versus nonoxygenated

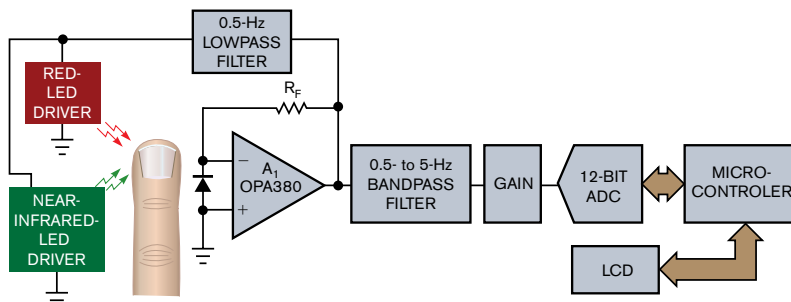


Figure 1 This pulse-oximeter circuit alternates the on-time of a red LED and a near-infrared LED to monitor oxygen saturation in the blood.

hemoglobin and your heart rate.

When you choose your device for the pulse-oximeter transimpedance-amplifier circuit, you need to make sure that the amplifier's input-bias current is very low or in a picoamp region at 25°C. The amplifier's input-bias current creates an output-voltage error by conducting through the high-impedance resistor, R<sub>F</sub>, in the amplifier's feedback loop. FET- or CMOS-amplifier input devices usually meet this requirement. A second consideration is that the low-frequency voltage noise of your amplifier must be very low. When you consider the input-voltage noise of the amplifier, scrutinize the impact of the flicker noise. After the transimpedance amplifier, a bandpass filter eliminates the noise above 5 Hz. Finally, the amplifier's initial offset error and overtemperature should be in the microvolt region if you want to minimize linearity errors. It may be worthwhile to use an autozero amplifier.

A normal output for the pulse oximeter is approximately 97%  $\pm$  2%, ranging from 95 to 100%. The alarms on the pulse oximeter usually sound when the SpO<sub>2</sub> level drops below 90%. If there is a shortage of oxygen in your system, you may experience poor judgment or loss of motor function. If a pulse oximeter indicates that your oxygen levels are stable, you may want to explore other diagnostic avenues, or perhaps you just dance to the beat of a different drummer. Good luck! EDN

### REFERENCES

- 1 *Medical Applications Guide*, pg 27, Texas Instruments, second quarter 2007, <http://focus.ti.com/lit/ml/slyb108b/slyb108b.pdf>.
- 2 Townsend, Neil, MD, "Pulse Oximetry," *Medical Electronics*, Michaelmas 2001, [http://courses.cs.tamu.edu/rgutier/cpsc483\\_s04/pulse\\_oximetry\\_notes.pdf](http://courses.cs.tamu.edu/rgutier/cpsc483_s04/pulse_oximetry_notes.pdf).

Bonnie Baker is a senior applications engineer at Texas Instruments. You can reach her at [bonnie@ti.com](mailto:bonnie@ti.com).