



Figure 1 This pulse-oximeter circuit alternates the on-time of a red LED and a near-infrared LED to monitor oxygen saturation in the blood.